



**JABATAN KEJURUTERAAN ELEKTRIK
PUSAT PENGAJIAN DIPLOMA (PPD), SPACE
UNIVERSITI TEKNOLOGI MALAYSIA
KUALA LUMPUR**

**ELECTRICAL ENGINEERING LABORATORY 2
(DDWE 2701)**

ELECTRONICS 1

**EXPERIMENT 2
ZENER REGULATOR**

EXPERIMENT 2 : ZENER REGULATOR

OBJECTIVES

At the end of this experiment, student should be able to understand the concept of regulation and can explain the operation of zener regulator.

EQUIPMENTS

1. DC power Supply
2. Multimeter
3. Transformer
4. Oscilloscope

COMPONENTS

1. Zener diode: 8 V, 1 W (2 units)
2. Resistor: 1 k Ω (1 unit), 2 k Ω (1 unit), 500 Ω (1 unit), 4 k Ω (1 unit) and Decade Resistor

Part A: Fix Power Supply (V_S) and Varies Load Resistances (R_L)

Procedure:

1. Make a connection as shown in Figure 1.
2. Set power supply to 15 V and varies load resistor (R_L) from 500 Ω , 1 k Ω , 3 k Ω , 6 k Ω , 8 k Ω and 10 k Ω .
3. Measure V_R , V_Z , V_L , I_S , I_L , I_Z for every changes of R_L and write the answer in Table A.
4. From Table A, plot load voltage (V_L) versus resistance (R_L) on the graph in Figure A.

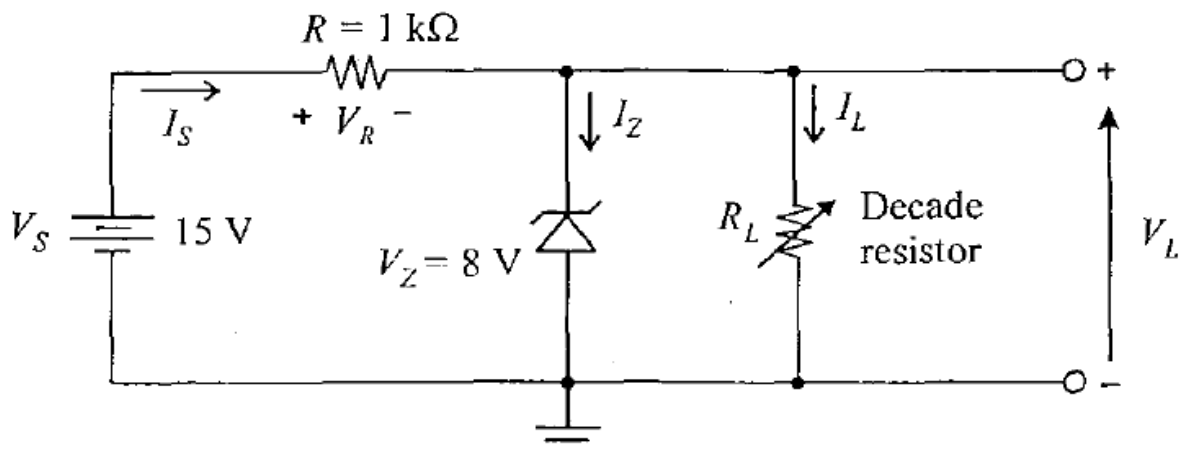


Figure 1

Part B: Fix Load Resistance (R_L) and Varies Power Supply (V_S).

Procedure:

1. Make a connection as shown in Figure 2.
2. Varies power supply from 4 V, 8 V, 15 V, 20 V, 22 V and 25 V. Load resistance (R_L) is fix to 2 k Ω .
3. Measure V_R , V_Z , V_L , I_S , I_L , I_Z for every changes of V_S and write the answer in Table B.
4. From Table B, plot load voltage (V_L) versus power supply (V_S) on the graph in Figure B.

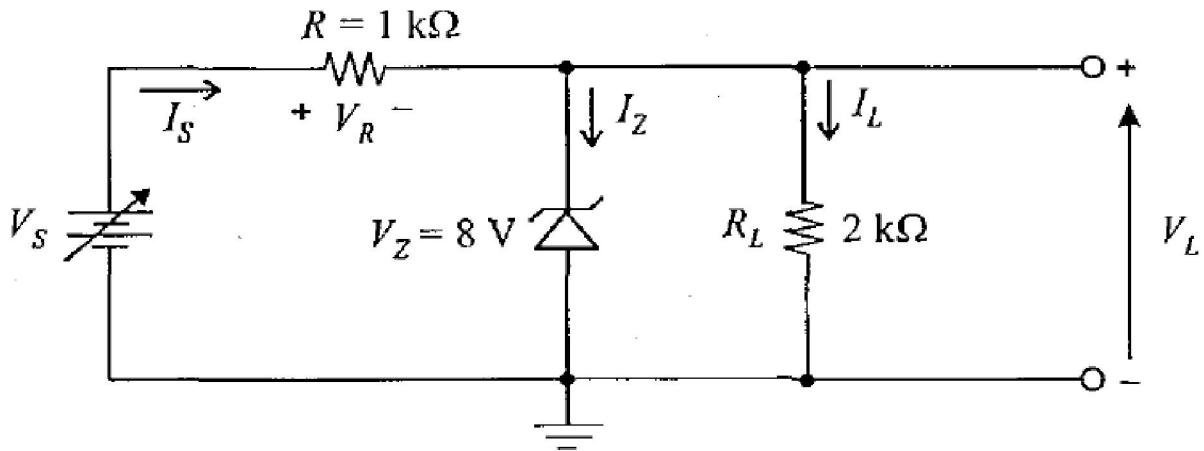


Figure 2

Part C

1. Make a connection as shown in Figure 3.
2. Connect Channel 1 Oscilloscope to $V_{\text{Secondary}}$ and Channel 2 to V_L . Plot $V_{\text{Secondary}}$ and V_L in Figure C in result sheet.

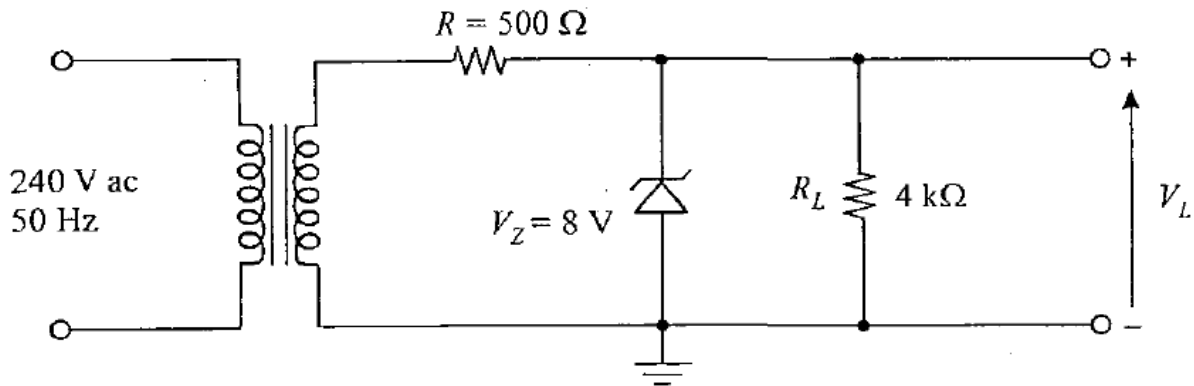


Figure 3

Part D

1. Make a connection as shown in Figure 4.
2. Connect Channel 1 Oscilloscope to $V_{\text{Secondary}}$ and Channel 2 to V_L . Plot $V_{\text{Secondary}}$ and V_L in Figure D in result sheet.

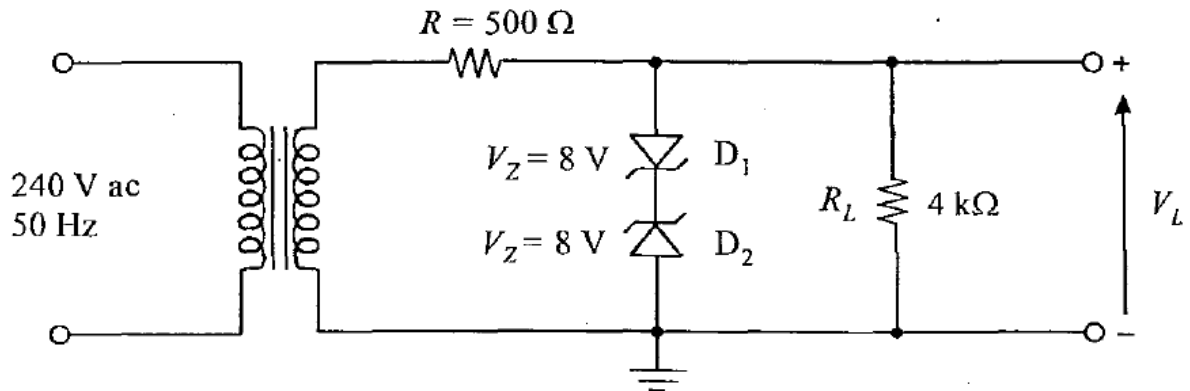


Figure 4