



**UTM**  
UNIVERSITI TEKNOLOGI MALAYSIA

Sekolah Pendidikan  
Profesional dan  
Pendidikan Berterusan  
(SPACE)

**JABATAN KEJURUTERAAN ELEKTRIK  
PUSAT PENGAJIAN DIPLOMA (PPD), SPACE  
UNIVERSITI TEKNOLOGI MALAYSIA  
KUALA LUMPUR**

**DDWE 1711 ELECTRICAL ENGINEERING LABORATORY 1  
(CIRCUIT THEORY 1)**

**THEORY & PRELIMINARY LABORATORY 3  
THE SUPERPOSITION AND THEVENIN'S THEOREM**

<b>Student name</b>	:	
<b>Lecturer</b>	:	
<b>Date</b>	:	

<b>No.</b>	<b>PO</b>	<b>CO</b>	<b>Student Marks</b>	<b>Marks</b>
<b>1</b>	<b>PO1</b>	<b>CO1</b>		<b>/15</b>

**Submit the completed preliminary report to the lecture in the lab before the lab session starts.**

## THEORY

### THE SUPERPOSITION THEOREM

Superposition is a method to determine the voltages and currents in a circuit that has many sources. It allows the calculation of the combined effect of many sources by looking at the individual effects of each source acting alone.

Each source is treated one at a time, as if it were the only ACTIVE source in the circuit. All the other sources are considered NOT ACTIVE; whereby voltage sources are replaced by short circuits, and current sources are replaced by open circuits.

The voltage or current can be calculated by taking the components due to the first source acting alone. The calculations are repeated for each source in the circuit. When all the sources have been considered, the overall voltage or current is the algebraic sum of the individual voltage or current.

The superposition theorem will work for any number of sources as long as you are consistent in accounting for the direction of currents and the polarity of voltages.

### PRELIMINARY WORK

#### THE SUPERPOSITION THEOREM

1. Given a circuit with two ideal voltage sources as shown in Figure 1. Find  $I_1$  and  $V_3$  using superposition theorem.

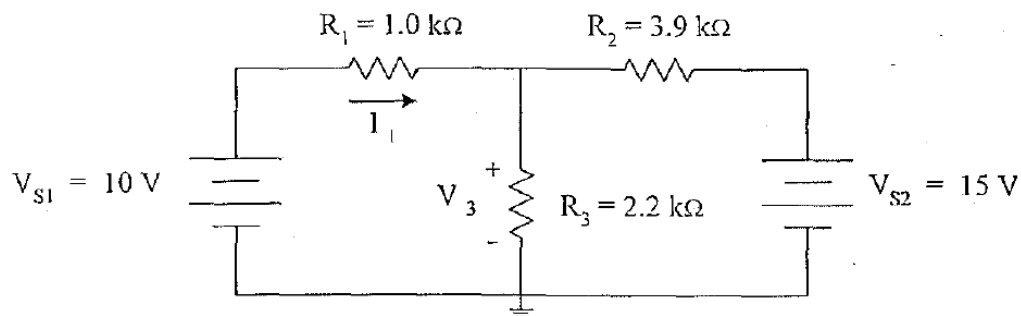


Figure 1


### Answer

PO1	CO1	.....	/4m
-----	-----	-------	-----


**THEORY**

**THE THEVENIN'S THEOREM**

The Thevenin's theorem provides a means of reducing a complicated, linear network into an equivalent circuit. The Thevenin equivalent circuit is composed of a voltage source in series with a resistor. To demonstrate this, we will apply the theorem to a simple three resistor circuit in Figure 2. According to the theorem, we should be able to replace the circuit to the left of terminal A-B with a Thevenin equivalent circuit as shown in Figure 3.

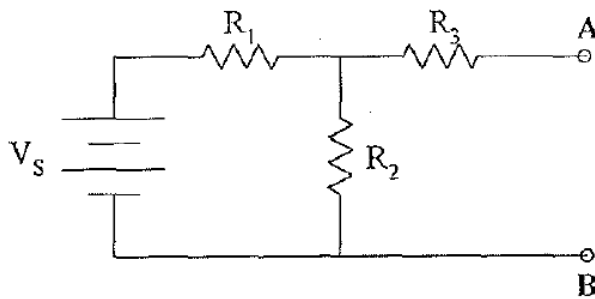

**Figure 2**

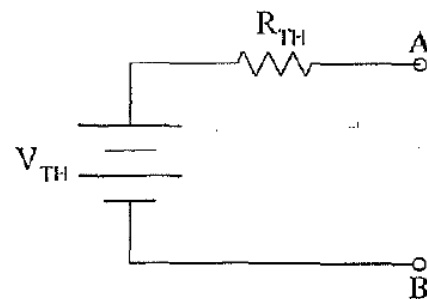


**Figure 3**

A device connected to the output (terminal A-B) is called a LOAD for the Thevenin circuit. If a load resistance  $R_L$  is connected across terminal A-B in both circuits of Figure 2 and Figure 3, the current flowing into  $R_L$  will be the same.

**PRELIMINARY WORK**

**THE THEVENIN'S THEOREM**

1. Referring to the circuit shown in Figure 4, calculate the current,  $I_L$  flowing through  $R_L$  for  $R_L = 2.2 \text{ k}\Omega$ . (Hint: solve by reducing the circuit to find the total resistance and the total current.)

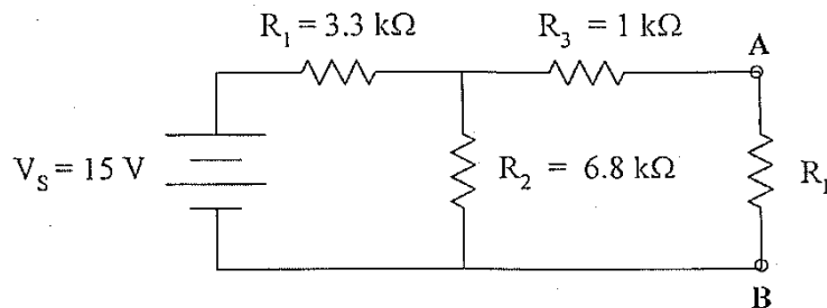

**Figure 4**

**Answer**

<b>PO1</b>	<b>CO1</b>	.....	<b>/4m</b>
------------	------------	-------	------------

2. Referring to Figure 4, find  $I_L$  flowing through  $R_L$  for  $R_L = 2.2 \text{ k}\Omega$  using Thevenin's Theorem.

<b>PO1</b>	<b>CO1</b>	.....	<b>/4m</b>
------------	------------	-------	------------

3. What can you conclude from the value of current,  $I_L$  obtained in Step 1 and Step 2.

.....

.....

.....

.....

.....

.....

<b>PO1</b>	<b>CO1</b>	.....	<b>/3m</b>
------------	------------	-------	------------