



**JABATAN KEJURUTERAAN ELEKTRIK
PUSAT PENGAJIAN DIPLOMA (PPD), SPACE
UNIVERSITI TEKNOLOGI MALAYSIA
KUALA LUMPUR**

**DDWE 1711 ELECTRICAL ENGINEERING LABORATORY 1
(CIRCUIT THEORY 1)**

**EXPERIMENT 3
THE SUPERPOSITION AND THEVENIN'S THEOREM**

Group members	1. 2. 3. 4. 5.
Lecturer	:
Date	:

No.	PO	CO	Student Marks	Marks
1	PO1	CO1		35%
2	PO2	CO4		40%
3	PO8	CO5		10%
Total Marks				/85%

EXPERIMENT 1 : THE SUPERPOSITION THEOREM & THEVENIN'S THEOREM'

OBJECTIVES

After doing this experiment; you will be able to:

1. construct a circuit with two voltage sources.
2. apply and verify the superposition theorem to linear circuits.
3. change a linear resistive network into all equivalent Thevenin circuit.
4. prove the equivalency of the resistive network with the Thevenin circuit.

APPARATUS

1. DC power supplies
2. Multimeter
3. Voltmeter
4. Ammeter (mA)
5. Decade resistance box

COMPONENTS

Resistors 1 k Ω , 2.2 k Ω , 3.3 k Ω , 3.9 k Ω , 6.8 k Ω .

INSTRUCTION

Show all calculations in the spaces provided in the Report Sheet.

PROCEDURE

PART 1 : THE SUPERPOSITION THEOREM

A : MEASUREMENT OF CURRENTS AND VOLTAGE IN CIRCUIT WITH TWO SOURCES

1. Obtain resistors listed in Table 1. Measure each resistor and record the measured values in Table 1.
2. Connect the circuit shown in Figure 1.

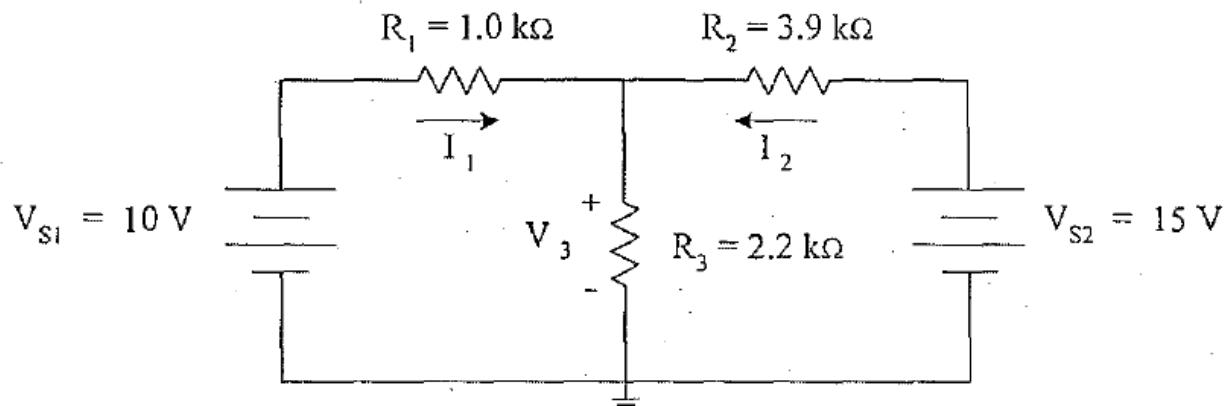


Figure 1

3. Switch on the power supplies. Measure the voltages across the power supplies using voltmeter. Adjust the voltage of the power supplies to the required values.
4. Use the ammeter to measure the currents, I_1 and I_2 . Record the values in Table 2.
(Note: Ammeter must be placed in **series** with the branch to be measured.)
5. Use the voltmeter to measure the voltage V_3 . Record the value in Table 2.

B : APPLYING THE SUPERPOSITION THEOREM

1. Use the same circuit as in Figure 1. Switch off the power supplies and remove the 15 V voltage source.
2. The 10 V, voltage source is made ACTIVE by replacing the 15 V voltage source with a jumper between the points labeled C and D, as shown in Figure 2.

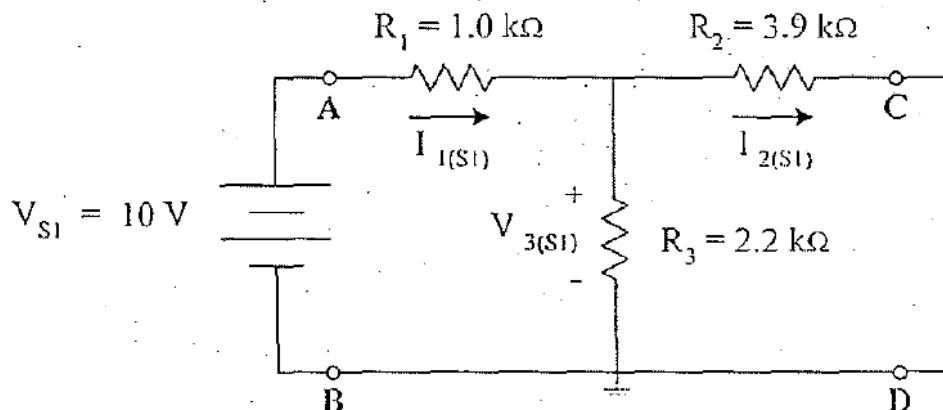


Figure 2

3. Switch on the 10 V voltage source.

4. Use the ammeter to measure the currents, $I_{1(SI)}$ and $I_{2(SI)}$. Record the values in Table 3.
5. Use the voltmeter to measure the voltage $V_{S(SI)}$. Record the value in Table 3.
6. Switch off the power supply.
7. Connect the circuit as shown in Figure 3. The 15 V voltage source is made ACTIVE by replacing the 10 V voltage source with a jumper between the points labeled A and B.

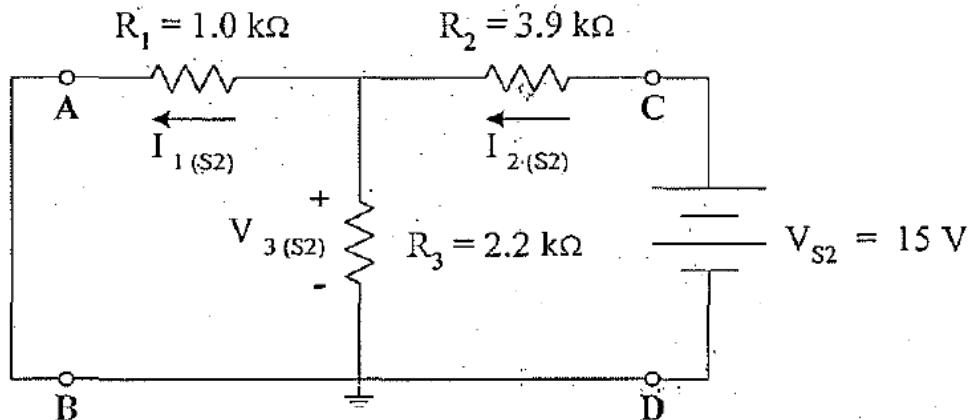


Figure 3

8. Switch on the 15 V, voltage source.
9. Use the ammeter to measure the currents, $I_{1(S2)}$ and $I_{2(S2)}$. Record the values in Table 3.
10. Use the voltmeter to measure the voltage $V_{3(S2)}$. Record the value in Table 3.
11. Calculate the algebraic sum of currents I_1 , I_2 and voltage V_3 in Table 3. Pay attention the direction of the currents. **Current in the same directions are added and currents in the opposite directions are subtracted.**

PART 2 : THE THEVENIN'S THEOREM

A : LINEAR RESISTIVE NETWORK

1. Obtain resistors listed in Table 4. Measure each resistor and record the measured values in Table 4.
2. Connect the circuit shown in Figure 4.

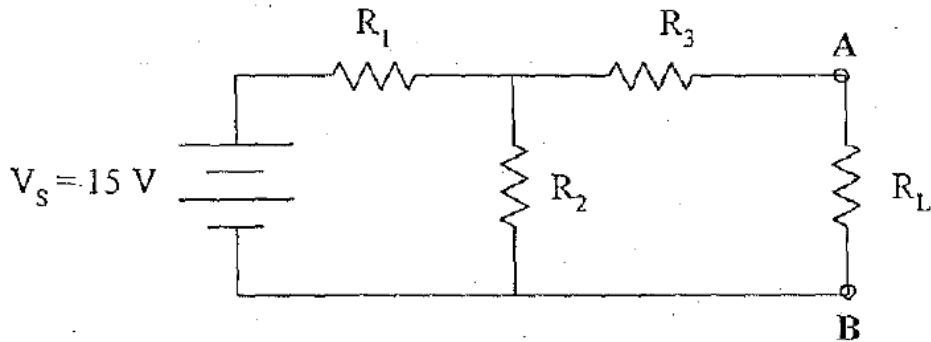


Figure 4

3. Switch on the power supply.
4. Use an ammeter to measure the current, I_L, flowing through the load resistor R_L. Record the value in Table 5.

B : THE THEVENIN'S THEOREM

1. Use the same circuit with the load resistor removed as shown in Figure 5.

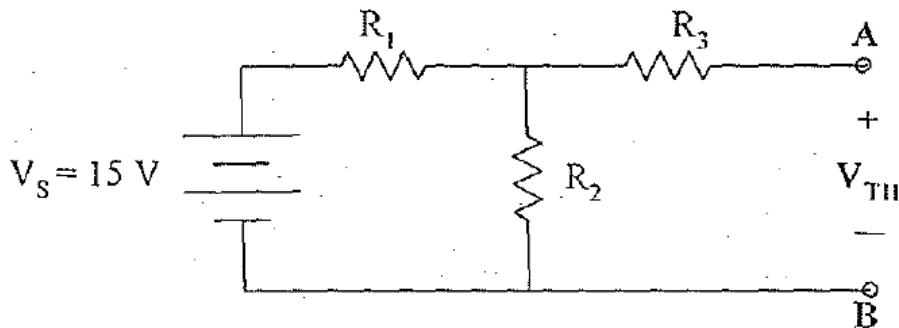


Figure 5

2. Measure the Thevenin equivalent voltage, V_{TH} across terminal A-B of Figure 5. Record the value in Table 6.
3. Disconnect the 15 V voltage source and replace it with a jumper (short circuit) as shown in Figure 6.

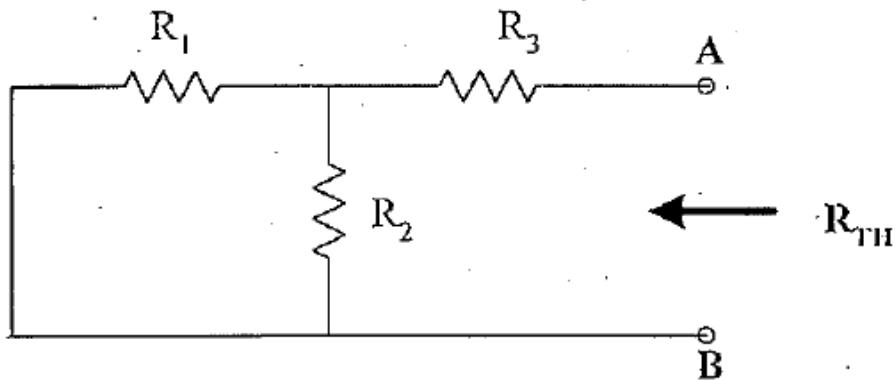


Figure 6

4. Measure the Thevenin equivalent resistance, R_{TH} looking from terminal A-B. Record the value in Table 6.
5. Draw the Thevenin equivalent circuit in the space provided in the report sheet:

C : THE THEVENIN EQUIVALENT CIRCUIT

1. Construct the Thevenin equivalent circuit obtained in Part B. Use the decade resistance box for the measured Thevenin equivalent resistance. The decade resistance box may not be accurate. Use your multimeter to set the resistance to the exact value.
2. Connect the load resistor R_L across the output terminal A-B.
3. Measure the current h flowing through the load resistor R_L . Record the value in Table 7.

RESULT AND REPORT

PART 1: SUPERPOSITION THEOREM

A : MEASUREMENT OF CURRENTS AND VOLTAGE IN CIRCUIT WITH TWO SOURCES

Table 1 (Step 1)

Resistor	Listed Value(kΩ)	Measured Value (kΩ)
R ₁	1.0	
R ₂	3.9	
R ₃	2.2	

PO1	CO1	/2m
-----	-----	-------	-----

Table 2 (Step 4 - 5)

Value	Measured Value
I ₁ (mA)	
I ₂ (mA)	
V ₃ (V)	

PO1	CO1	/2m
-----	-----	-------	-----

B : APPLYING THE SUPERPOSITION THEOREM

Table 3 (Steps 4 - 5, Step 9 - 10, Step 11)

V _{S1} active		V _{S2} active		Algebraic Sum	
I _{1(S1)}		I _{1(S2)}		I ₁ =I _{1(S1)} + I _{1(S2)}	
I _{2(S1)}		I _{2(S2)}		I ₂ =I _{2(S1)} + I _{2(S2)}	
V _{3(S1)}		V _{3(S2)}		V ₃ =V _{3(S1)} + V _{3(S2)}	

PO1	CO1	/3m
-----	-----	-------	-----

CONCLUSIONS:

.....
.....
.....
.....

PO1	CO1	/5m
------------	------------	-------	------------

PART 2: THE THEVENIN'S THEOREM

A : LINEAR RESISTIVE NETWORK

Table 4 (Step 1)

Resistor	Listed Value(kΩ)	Measured Value (kΩ)
R_1	3.3	
R_2	6.8	
R_3	1.0	
R_L	2.2	

PO1	CO1	/2m
------------	------------	-------	------------

Table 5 (Step 4)

I _L (mA)	
---------------------	--

PO1	CO1	/2m
------------	------------	-------	------------

B : THE THEVENIN'S THEOREM

Table 6 (Step 2 & Step 4)

V _{TH} (V)	
R _{TH} (kΩ)	

PO1	CO1	/2m
------------	------------	-------	------------

The Thevenin equivalent circuit (Step 5)

PO1	CO1	/5m
-----	-----	-------	-----

C: THE THEVENIN EQUIVALENT CIRCUIT

Table 7 (Step 3)

I _L (mA)	
---------------------	--

PO1	CO1	/2m
-----	-----	-------	-----

Comments on load current measured in Part 2A (Table 5) with the value obtained in Part 2C (Table 7)

.....
.....
.....
.....

PO1	CO1	/5m
-----	-----	-------	-----

CONCLUSIONS:

.....
.....
.....
.....

PO1	CO1	/5m
-----	-----	-------	-----

Guideline for ethic rubric (PO8):

ETHIC AND PROFESSIONAL MORAL (100 marks)					
Scale :	1 (5marks)	2 (10marks)	3 (15marks)	4 (20marks)	5 (25marks)
Criteria ✓ Understand the economic, environmental and socio-cultural impacts of professional practice	Very Poor	Poor	Moderate	Good	Excellent
A. Professional Practice (Punctuality/Follow the Rules)	Tidak menepati/ Tidak Mematuhi	Kurang menepati/ Kurang mematuhi	Adakala menepati / Adakala mematuhi	Menepati / Mematuhi	Sentiasa menepati / Sentiasa mematuhi
B. Ethical Behavior (Trustworthy / Respectfulness)	Tidak mengamalkan	Kurang mengamalkan	Adakala mengamalkan	Mengamalkan	Sentiasa mengamalkan
C. Social Cultural (Racial Harmony)	Tidak mengamalkan	Kurang mengamalkan	Adakala mengamalkan	Mengamalkan	Sentiasa mengamalkan
D. Sahsiah Rupa Diri	Tidak menepati	Kurang menepati	Adakala menepati	Menepati	Sentiasa menepati

PO8	CO5	/10%
-----	-----	-------	------

Guideline of practical skill rubric (PO2) :

Practical skill (100 marks)					
Scale :	1 (5marks)	2 (10marks)	3 (15marks)	4 (20marks)	5 (25marks)
Criteria ✓ Demonstrate the practical skill	Very Poor	Poor	Moderate	Good	Excellent
A. Circuit assembly/construction	5	10	15	20	25
B. Using appropriate measurement equipment and technique	5	10	15	20	25
C. Troubleshooting skill and technique	5	10	15	20	25
D. Follow lab regulation	5	10	15	20	25
	Total marks				

PO2	CO4	/40%
-----	-----	-------	------