



**JABATAN KEJURUTERAAN ELEKTRIK
PUSAT PENGAJIAN DIPLOMA (PPD), SPACE
UNIVERSITI TEKNOLOGI MALAYSIA
KUALA LUMPUR**

**ELECTRICAL ENGINEERING LABORATORY 2
(DDWE 2701)**

CIRCUIT THEORY 2

THEORY & PRELIMINARY LABORATORY 4

TWO PORT NETWORK

Student name	:	
Lecturer	:	
Date	:	

No.	PO	CO	Student Marks	Marks
1	PO1	CO1		/ 10

Submit the completed preliminary report to the lecturer in the lab before the lab session starts.

THEORY

A two port network as shown in Figure 1 is defined as a network having two pairs of terminals. known as terminals 1-1' and 2-2'. Current I_1 leaves terminal 1, enters the two-port network and exits at terminal 1'. Similarly, current I_2 , leaves terminal 2, enters the two-port network and exits at terminal 2'.

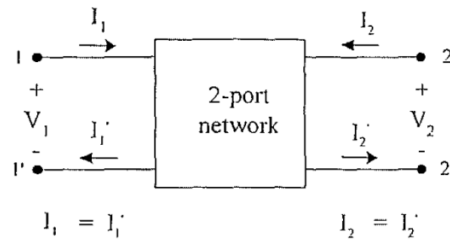


Figure 1

The parameters of the two port network describe the network behavior in terms of the voltage and current at each port. Four types of two-port parameters that are commonly used are impedance-parameter Z , admittance-parameter Y , hybrid-parameter and transmission-parameter, T or $ABCD$. The two-port network equations that relate the variables in the network are given below.

Z-parameters :

(1)

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \end{aligned}$$

Y-parameters:

(2)

$$\begin{aligned} I_1 &= y_{11} V_1 + y_{12} V_2 \\ I_2 &= y_{21} V_1 + y_{22} V_2 \end{aligned}$$

h-parameters :

(3)

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

ABCD-parameters:

(4)

$$\begin{aligned} V_1 &= A V_2 - B I_2 \\ I_1 &= C V_2 - D I_2 \end{aligned}$$

Z-parameters can be determined using open-circuit conditions at terminals 1-1' and 2-2'. When terminals 2-2' are opened, $I_2 = 0$, thereby using equation (1), Z_{11} and Z_{21} can be determined as follows:

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

When terminals 1-1' are opened, $I_1 = 0$, then by using equation (1), Z_{12} and Z_{22} can be determined as follows:

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} \quad Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

Y-parameters can be determined using short-circuit conditions at terminals 1-1' ($V_1=0$) and terminals 2-2' ($V_2=0$). To obtain h-parameters and ABCD-parameters, both short-circuit and open-circuit conditions are required. The equations for all the parameters are given in Attachment 1.

The T-network as shown in Figure 2 is the simplest form of a two port network. Z-parameters of the T-network can be simply determined using mesh analysis.

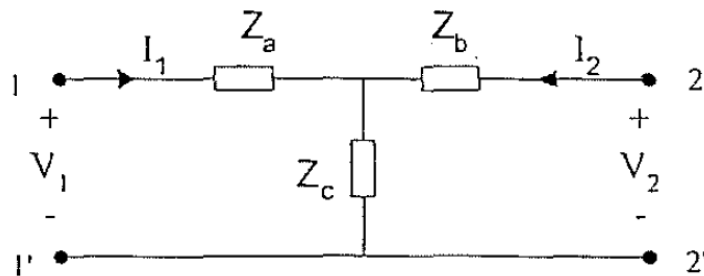


Figure 2 : T-network

Another form of a two-port network is the π -network as shown in Figure 3. Y-parameters of the π -network can be easily determined by using nodal analysis.

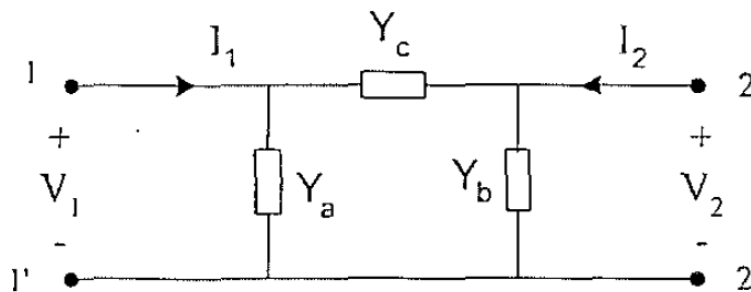


Figure 3 : π -network

PRELIMINARY WORK

1. Given a T-network as shown in Figure 4, determine the Z-parameters using mesh analysis.

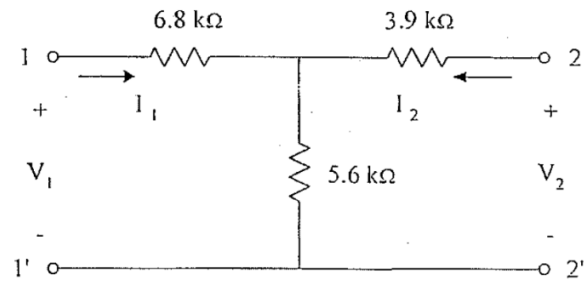


Figure 4

Answer

PO1	CO1	/5m
-----	-----	-------	-----

2. Given a π -network as shown in Figure 5, determine Y-parameters using node analysis.

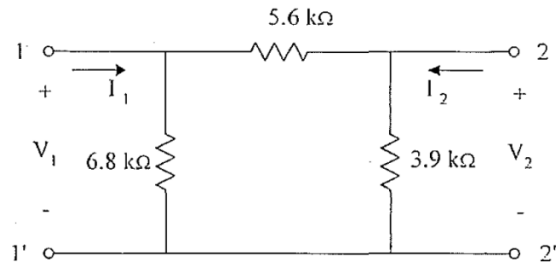


Figure 5

Answer

PO1	CO1	/5m
-----	-----	-------	-----

ATTACHMENT 1 : 2-PORT NETWORK PARAMETERS

Z - parameters

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2 = 0} \quad z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2 = 0} \quad z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1 = 0} \quad z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1 = 0}$$

Y-parameters

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2 = 0} \quad y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2 = 0} \quad y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1 = 0} \quad y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1 = 0}$$

h-parameters

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2 = 0} \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2 = 0} \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1 = 0} \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1 = 0}$$

ABCD-parameters

$$A = \left. \frac{V_1}{V_2} \right|_{I_2 = 0} \quad B = \left. \frac{-V_1}{I_2} \right|_{V_2 = 0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2 = 0} \quad D = \left. \frac{-I_1}{I_2} \right|_{V_2 = 0}$$