



Instruction

DIMMER → Control L1

DOOR BELL SWITCH = S1

S2 & S3 IS TWO-WAY SWITCH CONTROL L2

FIGURE 3