



### Instruction

- S1 and S2 is the two-way switches control lights L1 and L2.
- S3 is a one-way switches with fan regulator to control points K1(Fan)
- Points L1, L2 and K1 should use batten holder provided.
- Use radial circuit to install socket outlet.