



**UTM**  
UNIVERSITI  
TEKNOLOGI MALAYSIA

Sekolah Pendidikan  
Profesional dan  
Pendidikan Berterusan  
(SPACE)

**JABATAN KEJURUTERAAN ELEKTRIK  
PUSAT PENGAJIAN DIPLOMA (PPD), SPACE  
UNIVERSITI TEKNOLOGI MALAYSIA  
KUALA LUMPUR**

**DDWE 3711 ELECTRICAL ENGINEERING  
LABORATORY  
(INDUSTRIAL ELECTRONICS)**

**EXPERIMENT 3  
SCR PHASE CONTROL CIRCUITS**

## **OBJECTIVE**

To understand the operation of the SCR as a power control device.

## **Learning Outcomes**

At the end of the experiment, students must be able to:

Test SCR using a multi-meter.

Connect a circuit from the schematic drawing given.

Use the oscilloscope to display the waveforms from the circuit.

Sketch and label the waveforms across the SCR and load from a circuit.

Identify the triggering and conduction angle.

Make a record of the results obtained from the experiment.

## **List of Equipment and Components**

Oscilloscope

SCR

Bulb

1  $\Omega$  5 W resistor

4.7 k $\Omega$  resistor

1 k $\Omega$  potentiometer

1  $\mu$ F capacitor

10  $\mu$ F capacitor

## **METHODS**

### **PART A: Identifying the terminals of the SCR**


Refer to SCR data sheet:

1. Determine the SCR terminals: anode, cathode and gate.
2. Sketch the physical structure of the SCR and label the terminals.

### **PART B: Testing the SCR**

1. With the multimeter in the highest ohm range. Connect the positive terminal of the meter to the anode and negative terminal to the cathode.
  - a. With the gate open, measure and record the resistance of the SCR.
  - b. Short the gate to the anode, measure and record the resistance of the SCR.
2. Reverse the connections of the meter, with the anode to the negative and cathode to the positive.
  - a. With the gate open, measure and record the resistance of the SCR.
  - b. Short the gate to the anode, measure and record the resistance of the SCR.


**PART C: 90° Phase Control Circuit**

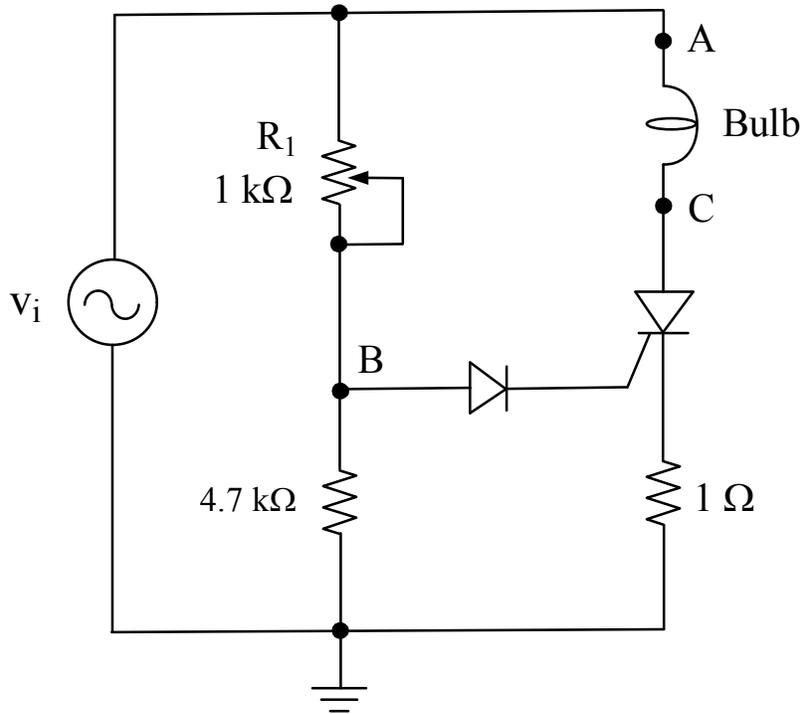

**Figure 1**

1. Construct the circuit as in Figure 1.  $V_{in} = 6 V_p$ .
2. Connect CHI of the oscilloscope to point A and CH2 to point B.
3. Vary the 1 kΩ potentiometer, observe the variation of the voltage waveforms of point A and B and the variation of the brightness of the lamp.
4. Set the potentiometer so that the SCR is triggering at the minimum firing angle.
  - a. Sketch and label the waveform of point A and B.
  - b. Calculate the minimum firing angle.
  - c. Measure the resistance of the potentiometer.
  - d. Connect CHI of the oscilloscope to point A and CH2 to point C. Sketch and label the waveform of point A and C.
5. Repeat step 4 for the maximum firing angle.
6. Compare the results of waveforms obtained from the experiment.

**PART C: 180° Phase Control Circuit**

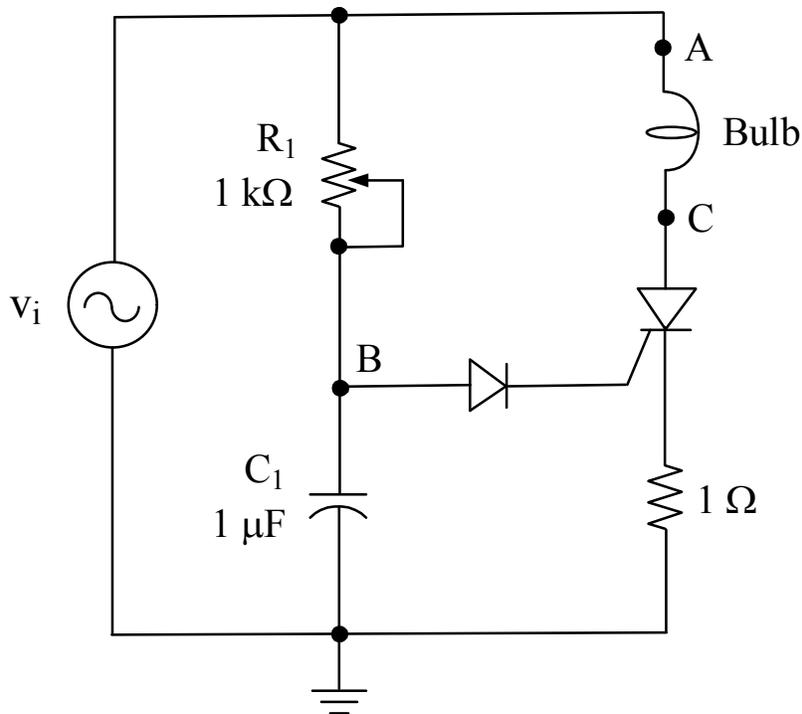

**Figure 2**

1. Construct the circuit as in Figure 2.  $V_{in} = 6 V_p$ .
2. Connect CH1 of the oscilloscope to point A and CH2 to point B.
3. Set the potentiometer so that the SCR is triggering at the minimum firing angle.
  - a. Sketch and label the waveform of point A and B.
  - b. Calculate the minimum firing angle.
  - c. Measure the resistance of the potentiometer.
  - d. Connect CH1 of the oscilloscope to point A and CH2 to point C. Sketch and label the waveform of point A and C.
4. Repeat step 3 for the maximum firing angle.
5. Compare the results of waveforms obtained from the experiment.
6. Change  $C = 10 \mu f$  and repeat Step 3 and Step 4.



**UTM**  
UNIVERSITI  
TEKNOLOGI MALAYSIA

Sekolah Pendidikan  
Profesional dan  
Pendidikan Berterusan  
(SPACE)

**JABATAN KEJURUTERAAN ELEKTRIK  
PUSAT PENGAJIAN DIPLOMA (PPD), SPACE  
UNIVERSITI TEKNOLOGI MALAYSIA  
KUALA LUMPUR**

**DDWE 3711 ELECTRICAL ENGINEERING  
LABORATORY  
(INDUSTRIAL ELECTRONICS)**

**REPORT SHEET 3  
SCR PHASE CONTROL CIRCUITS**

<b>Group members</b>	1.
	2.
	3.
<b>Lecturer</b>	:
<b>Date</b>	:

<b>No.</b>	<b>PO</b>	<b>CO</b>	<b>Student marks</b>	<b>Marks</b>
<b>1</b>	<b>PO1</b>	<b>CO5</b>		<b>60%</b>
<b>2</b>	<b>PO2</b>	<b>CO5</b>		<b>20%</b>
<b>3</b>	<b>PO4</b>	<b>CO5</b>		<b>10%</b>
<b>4</b>	<b>PO8</b>	<b>CO5</b>		<b>10%</b>
<b>Total marks</b>				<b>100%</b>

**EXPERIMENT 1: SCR PHASE CONTROL CIRCUITS**

**PART A: Identifying the terminals of the SCR**

Sketch the physical structure of the SCR and label the terminals.

PLO1	CLO5	..... / 2 m
------	------	-------------

**PART B: Testing the SCR**

1. With the multimeter in the highest ohm range. Connect the positive terminal of the meter to the anode and negative terminal to the cathode.
  - a. With the gate open, measure and record the resistance of the SCR.  
\_\_\_\_\_
  - b. Short the gate to the anode, measure and record the resistance of the SCR.  
\_\_\_\_\_
  
2. Reverse the connections of the meter, with the anode to the negative and cathode to the positive.
  - a. With the gate open, measure and record the resistance of the SCR.  
\_\_\_\_\_
  - b. Short the gate to the anode, measure and record the resistance of the SCR.  
\_\_\_\_\_

PLO1	CLO5	..... / 2 m
------	------	-------------

**PART C: 90° Phase Control Circuit**

Vary the 1 kΩ potentiometer, observe the variation of the voltage waveforms at point A and B and the variation of the brightness of the lamp. State the observation.

---



---



---



---


PLO1	CLO5	..... / 2 m
------	------	-------------

Minimum firing angle (Calculated)	Resistance of potentiometer (kΩ) (Measured)

**Table 1**

PLO1	CLO5	..... / 1 m
------	------	-------------


Sketch and label the waveform of point A and B (**Minimum firing angle**)

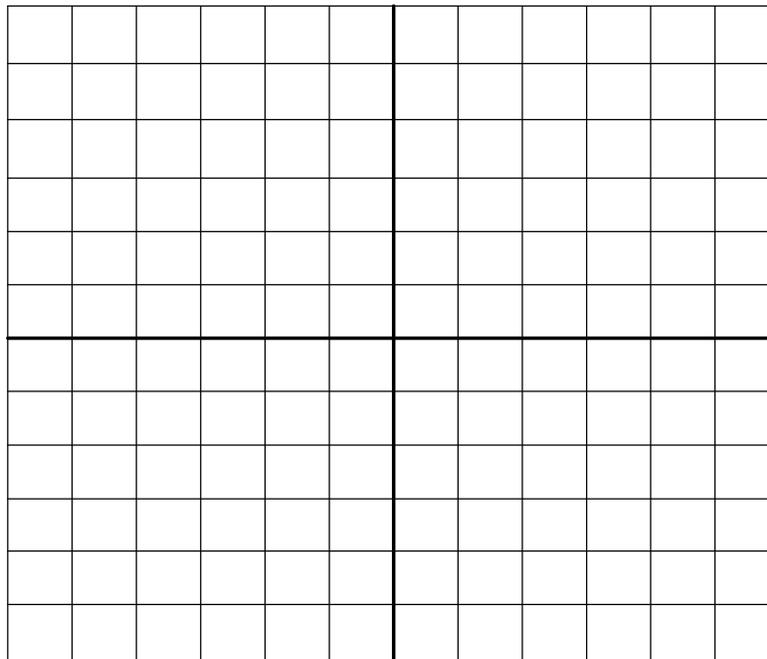

**Figure 1**

PLO1	CLO5	..... / 3 m
------	------	-------------

Sketch and label the waveform of point A and C (**Minimum firing angle**)

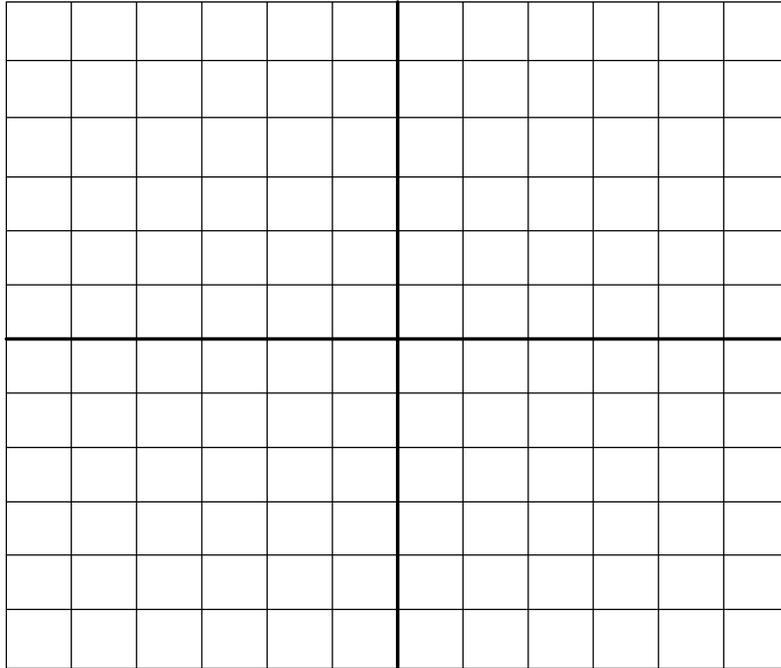

**Figure 2**

PLO1	CLO5	..... / 2 m
------	------	-------------

Compare and write a conclusion based on the result of **Table 1**, **Figure 1** and **Figure 2**.

---

---

---

---

---

---

---

---


PLO1	CLO5	..... / 3 m
------	------	-------------

Maximum firing angle (Calculated)	Resistance of potentiometer (k $\Omega$ ) (Measured)

**Table 2**

PLO1	CLO5	..... /1 m
------	------	------------


Sketch and label the waveform of point A and B (**Maximum firing angle**)

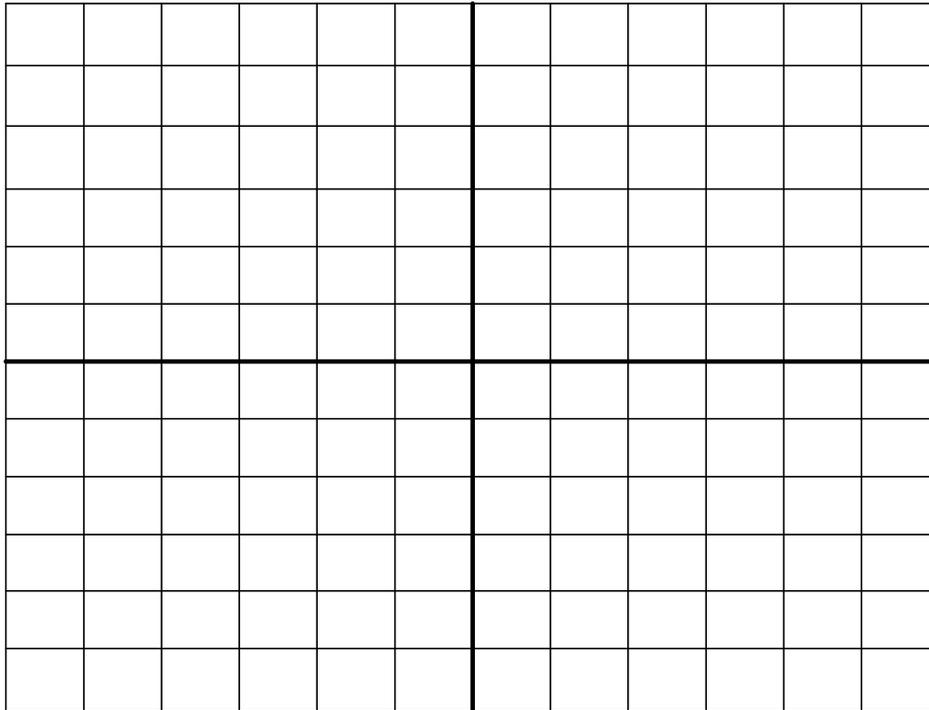

**Figure 3**

PLO1	CLO5	..... / 3 m
------	------	-------------

Sketch and label the waveform of point A and C (**Maximum firing angle**)

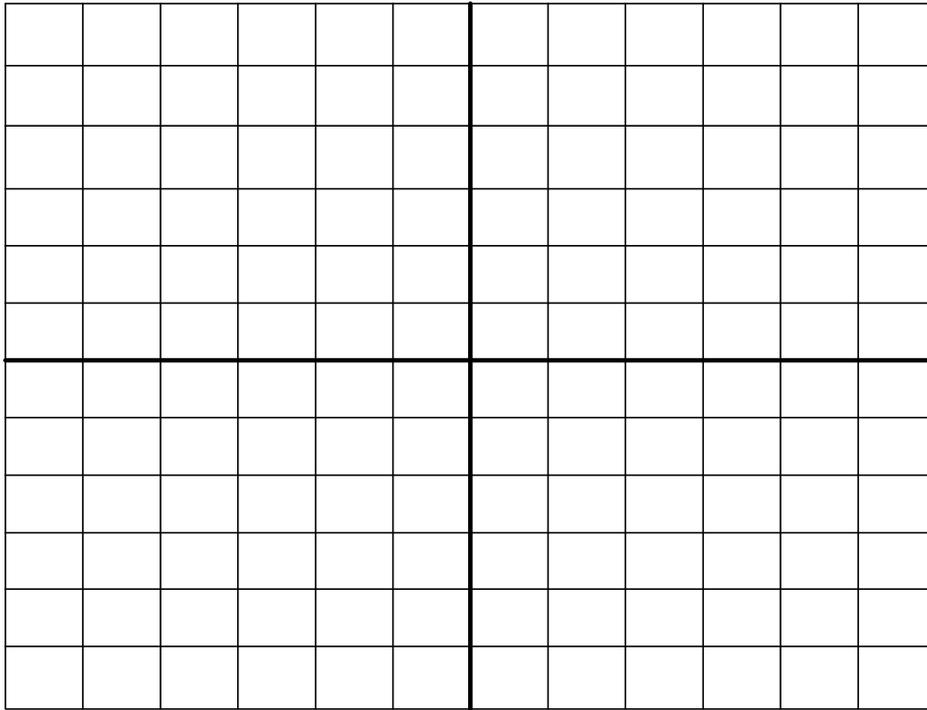

**Figure 4**

PLO1	CLO5	..... / 2 m
------	------	-------------

Compare and write a conclusion based on the result of **Table 2**, **Figure 3** and **Figure 4**.

---

---

---

---

---

---

---

---

PLO1	CLO5	..... / 3 m
------	------	-------------


**PART C: 180° Phase Control Circuit, C = 1 μF**

Minimum firing angle (Calculated) C = 1 μF	Resistance of potentiometer (kΩ) (Measured) C = 1 μF

**Table 3**

PLO1	CLO5	..... / 1 m
------	------	-------------


Sketch and label the waveform of point A and B (**Minimum firing angle**), C = 1 μF

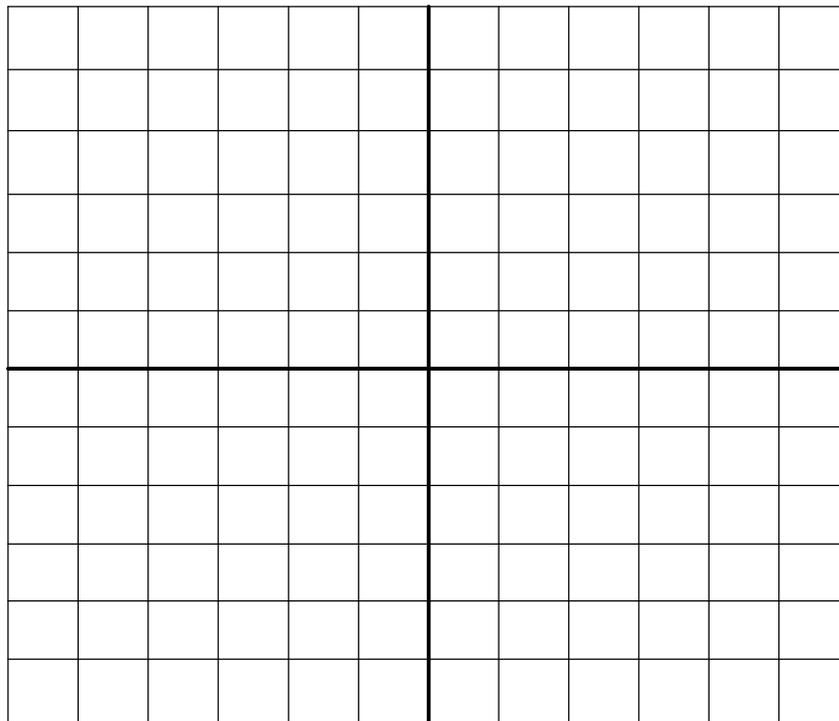

**Figure 5**

PLO1	CLO5	..... / 3 m
------	------	-------------

Sketch and label the waveform of point A and C (**Minimum firing angle**),  $C = 1 \mu\text{F}$

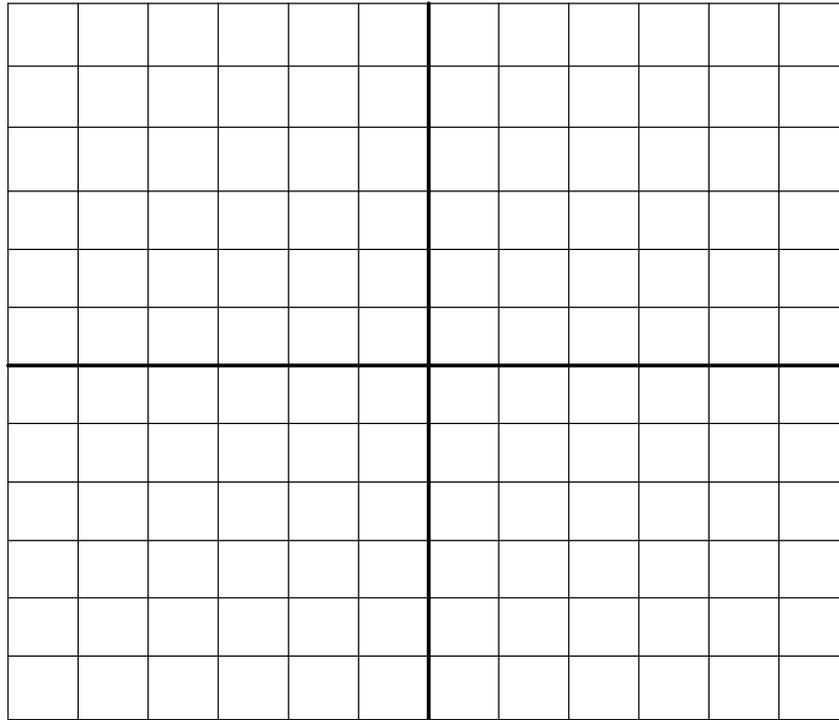

**Figure 6**

PLO1	CLO5	..... / 2 m
------	------	-------------

Compare and write a conclusion based on the result of **Table 3**, **Figure 5** and **Figure 6**.

---

---

---

---

---

---

---

---


PLO1	CLO5	..... / 3 m
------	------	-------------

Maximum firing angle (Calculated) C = 1 $\mu$ F	Resistance of potentiometer (k $\Omega$ ) (Measured) C = 1 $\mu$ F

**Table 4**

PLO1	CLO5	..... / 1 m
------	------	-------------


Sketch and label the waveform of point A and B (**Maximum firing angle**), C = 1  $\mu$ F

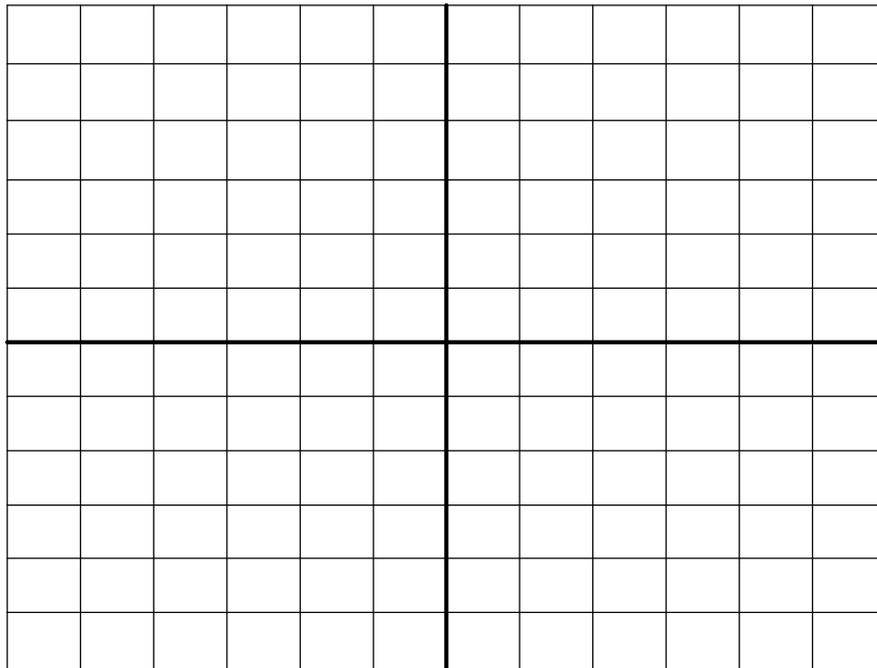

**Figure 7**

PLO1	CLO5	..... / 3 m
------	------	-------------

Sketch and label the waveform of point A and C (**Maximum firing angle**),  $C = 1 \mu\text{F}$

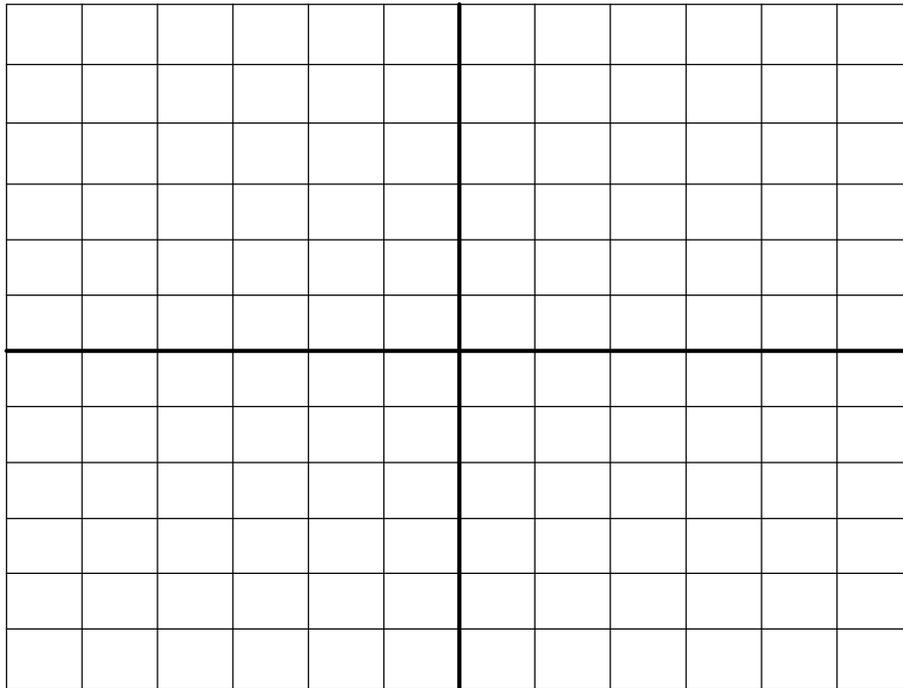

**Figure 8**

PLO1	CLO5	..... / 2 m
------	------	-------------

Compare and write a conclusion based on the result of **Table 4**, **Figure 7** and **Figure 8**.

---



---



---



---



---



---



---

PLO1	CLO5	..... / 3 m
------	------	-------------


**PART C: 180° Phase Control Circuit, C = 10 μF**

Minimum firing angle (Calculated) C = 10 μF	Resistance of potentiometer (kΩ) (Measured) C = 10 μF

**Table 5**

PLO1	CLO5	..... / 1 m
------	------	-------------


Sketch and label the waveform of point A and B (**Minimum firing angle**), C = 10 μF

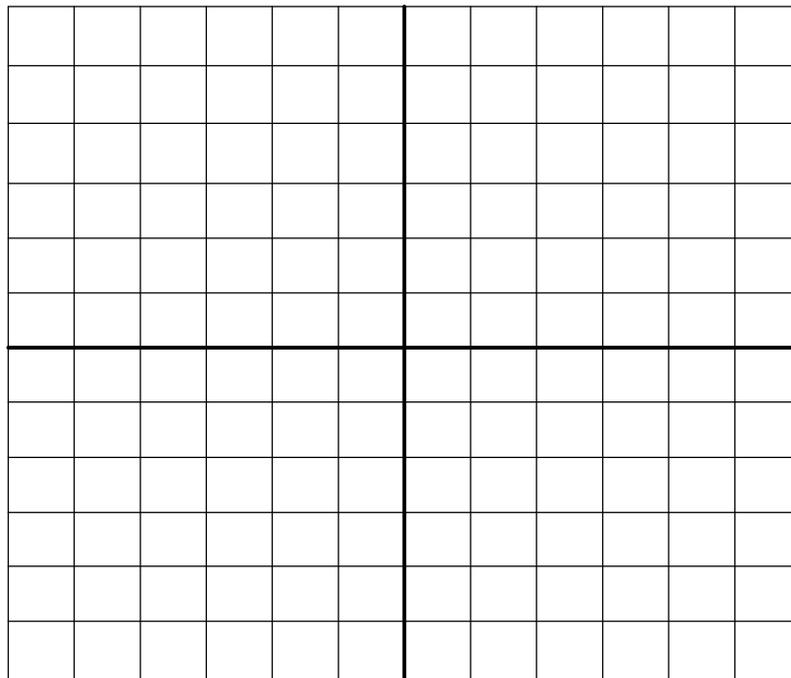

**Figure 9**

PLO1	CLO5	..... / 3 m
------	------	-------------

Sketch and label the waveform of point A and C (**Minimum firing angle**),  $C = 10 \mu\text{F}$

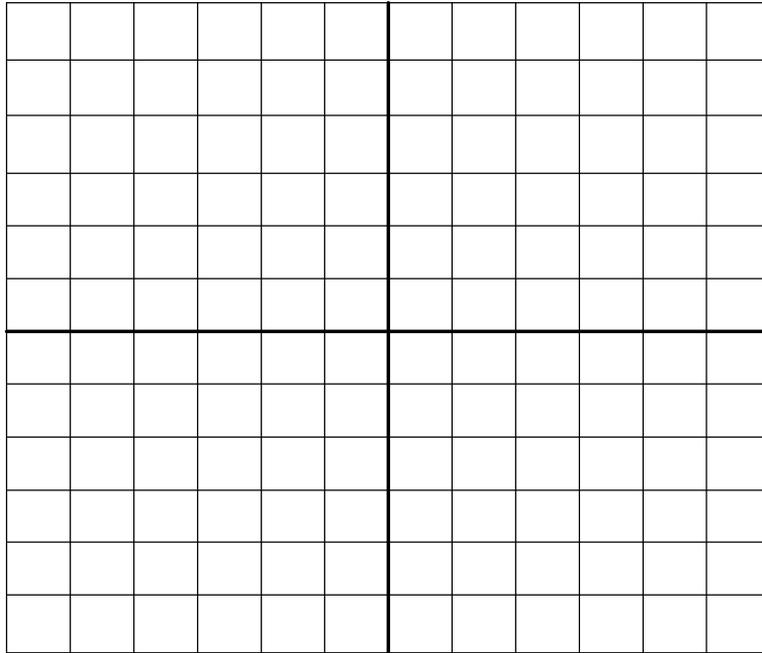

**Figure 10**

PLO1	CLO5	..... / 2 m
------	------	-------------

Compare and write a conclusion based on the result of **Table 5**, **Figure 9** and **Figure 10**.

---

---

---

---

---

---

---

---


PLO1	CLO5	..... / 3 m
------	------	-------------

Maximum firing angle (Calculated) C = 10 $\mu$ F	Resistance of potentiometer (k $\Omega$ ) (Measured) C = 10 $\mu$ F

**Table 6**

PLO1	CLO5	..... / 1 m
------	------	-------------


Sketch and label the waveform of point A and B (**Maximum firing angle**), C = 10  $\mu$ F

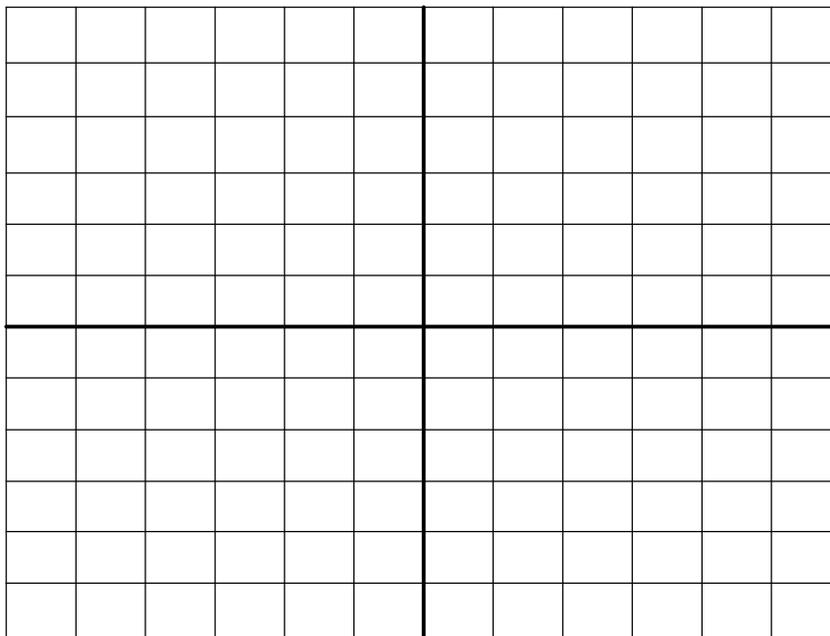

**Figure 11**

PLO1	CLO5	..... / 3 m
------	------	-------------

Sketch and label the waveform of point A and C (**Maximum firing angle**),  $C = 10 \mu F$

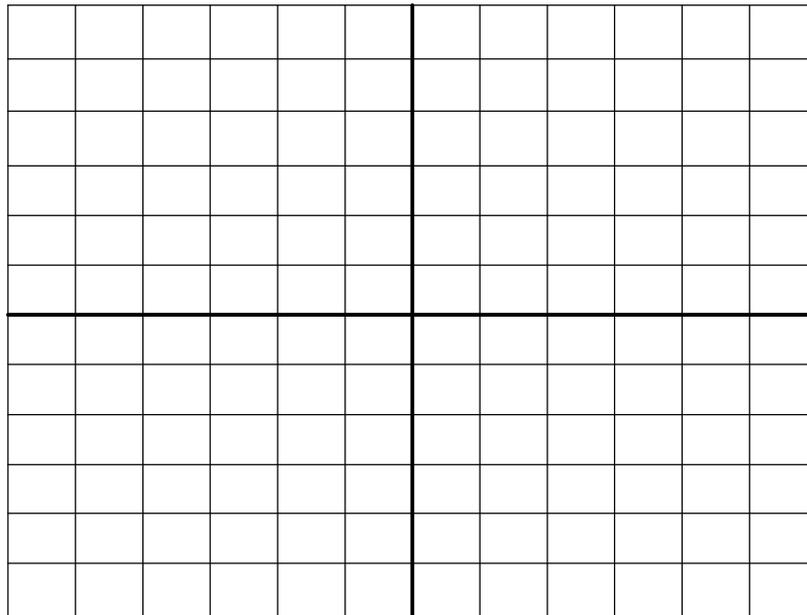

**Figure 12**

PLO1	CLO5	..... / 2 m
------	------	-------------

Compare and write a conclusion based on the result of **Table 6**, **Figure 11** and **Figure 12**.

---

---

---

---

---

---

---

---

PLO1	CLO5	..... / 3 m
------	------	-------------

**PLO2 (Psychomotor/Hands on Skill)**

Criteria	Very poor (5 Marks)	Poor (10 Marks)	Moderate (15 Marks)	Good (20 Marks)	Excellent (25 Marks)
<b>Ability to perform lab works based on the manual/ guidelines provided</b>	Not at all	Quite Limited /Selectively	Can perform lab work moderately but require a lot of guidance	Can perform lab work systematically and only need minor guidance	Demonstrate systematic and excellent performances
<b>Ability to perform simple lab work without supervision</b>	Need full supervision	Major supervision	Minor supervision	Limited supervision	Work independently With no supervision
<b>Ability to carry out lab work efficiently on the following criteria, (circuit assembly, using measurement apparatus and techniques)</b>	Not able to construct a full circuit, poor/inaccurate measurement techniques/usage of equipment	Completed full circuit but poor/inaccurate measurement techniques/usage of equipment	Completed full circuit and it works successfully. However the measurement techniques/usage of equipment had some minor deficiency	Completed full circuit and it works successfully. However the measurement techniques/usage of equipment had produced a few errors/corrections.	Circuit was completed and works properly without any errors /corrections. Also demonstrated an excellent skills/conducts.
<b>Ability to collect the required data, performs appropriate analysis and/or troubleshooting (if necessary).</b>	Not able to collect data and/or perform analysis	Limited data collection but not able to perform analysis/ troubleshooting	Demonstrates major errors in data collection and /or analysis. Limited ability in troubleshooting	Minor error in data collection and analysis. Good approach/techniques in troubleshooting.	Data collection and data analysis are done systematically and performs excellent approaches to trouble shoot (if necessary)

**PLO4 for Laboratory Report**

Criteria	VERY POOR (5)	POOR (10)	MODERATE (15)	GOOD (20)	EXCELLENT (25)
<b>Data Collection</b>	No data reported.	Data is brief and missing significant pieces of information .	Incomplete these of components of data (Both tables and Graphs): <ul style="list-style-type: none"> <li>• _____ Tables</li> <li>• _____ Graphs</li> </ul>	Only one component of data is incomplete (either table or graph). <ul style="list-style-type: none"> <li>• Tables/Graphs</li> </ul>	Data is completed properly and attributes mentioned below are observed with great care: <ul style="list-style-type: none"> <li>• Tables are easy to read and units are provided.</li> <li>• Graphs are labeled and shown trends.</li> </ul>
<b>Completing/ Answering Questions</b>	Questions are not answered at all.	Attempts were made but gave wrong answer to every question.	Questions are answered without any depth and with many errors.	Questions are properly answered but with a few errors.	Questions are answered completely and correctly.
<b>Summary/ Conclusion</b>	No conclusion or summary is/are drawn/reported	Conclusion is too brief without any reference to important pieces of information	Any two components of the conclusion/summary (mentioned) are missing : <ul style="list-style-type: none"> <li>• Summary</li> <li>• Data</li> <li>• Hypothesis</li> <li>• Errors</li> </ul>	Any component of the conclusion /Summary (mentioned) is missing: <ul style="list-style-type: none"> <li>• Summary</li> <li>• Data</li> <li>• Hypothesis</li> <li>• Errors</li> </ul>	Conclusion /Summary of these attributes below were addressed/reported properly, clearly and systematically. <ul style="list-style-type: none"> <li>• experiment,</li> <li>• data cited</li> <li>• hypothesis/assumptions made</li> <li>• The source of errors.</li> </ul>
<b>Report Quality</b>	No attention to detail evident.	Report contains many errors.	Report is good but with few spelling or grammatical errors.	Report is well written and cohesive, with a few errors	Report is very well written without any spelling or grammatical mistakes.

**PLO8**

Criteria	Very poor (5 Marks)	Poor (10 Marks)	Moderate (15 Marks)	Good (20 Marks)	Excellent (25 Marks)
<b>Professional Practice (Punctuality/Follow the Rules)</b>	Non- Conforming/ Not punctual	Not always Conforming/ Not always punctual	Sometimes Conforming/ Sometimes punctual	Conforming /Punctual	Always Conforming /Always Punctual
<b>Ethical Conduct/Behaviour (Trustworthy / Respectfulness)</b>	Does not practice	Not always practicing	Sometimes only	Mostly practicing	Always practicing
<b>Social Cultural (Racial Harmony)</b>	Does not observe	Not always observe	Sometimes observe	Mostly observe	Always observe
<b>Personality</b>	Mostly unpleasant	Not always pleasant	Moderately pleasant	Mostly pleasant	Always pleasant